



Redraw the given circuit using only the given AND gates, OR gates and INVERTERS. Additional gates and inverters are not allowed

