

16.265 Logic Design
 Experiment 4:: Counter - JK flip-flops
 Name: Harsh Patel
 Student Logic Number: 209
 Counter sequence: 163402

